


# DC/DC Converter Application Information

IC Product Name	BD9E102FJ	
Topology	Buck (Step-Down) Switching Regulator	
Туре	Non-Isolation	

	Input	Output		
1	7.2V to 26V	5.0V, 1A		

BD9E102FJ Application Note

## Typical Application Circuit

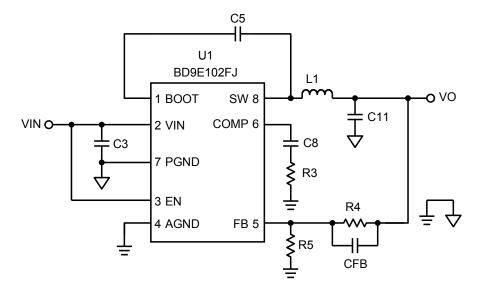

## ■ EN terminal setting (3-pin)

Terminal state	IC operation
≥ 2.5V	Normal operation
≤ 0.8V	Power down

## Output voltage setting

$$V_{OUT} = \frac{R_4 + R_5}{R_5} \times 1.0 \ [V]$$

Input/output voltage conditions are required to satisfy the following equations:

$$V_{OUT} = (V_{IN} \times 0.143) V \sim (V_{IN} \times 0.7) V$$

$$(V_{IN} \times 0.143) \ge 1.0V$$

#### Bill of Materials

#### 1. V<sub>O</sub>=5.0V (V<sub>IN</sub>=7.2V to 26V)

Count	Reference Designator	Туре	Value	Description	Manufacturer Part Number	Manufacturer	Configuration (mm)
1	C3	Ceramic Capacitor	10μF	50V, B, ±10%	GRM32EB31H106KA12	MURATA	3225
1	C5	Ceramic Capacitor	0.1µF	25V, B, ±20%	GRM155B31E104MA87	MURATA	1005
1	C8	Ceramic Capacitor	2200pF	25V, B, ±10%	GRM155B11E222KA01	MURATA	1005
1	C11	Ceramic Capacitor	22µF	10V, B, ±10%	GRM31CB31A226KE19	MURATA	3216
1	CFB	Ceramic Capacitor	33pF	25V, CH, ±5%	GRM1552C1E330JA01	MURATA	1005
	L1	Inductor	6.8µH	±30%, DCR=52mΩmax, 2.3A	MSS6132-682ML	Coilcraft	6161
				±30%, DCR=99.6mΩmax, 2.5A	LQH5BPN6R8NT0	Murata	5050
				±20%, DCR=82.6mΩmax, 2.2A	CDRH4D22HPNP-4R7NC	Sumida	4747
				±20%, DCR=55.9mΩmax, 2.6A	NRS6028T6R8MMGJV	TAIYO YUDEN	6060
1				±20%, DCR=67.6mΩmax, 2.5A	NRS5030T6R8MMGJV	TAIYO YUDEN	4949
				±30%, DCR=35.1mΩmax, 2.1A	CLF6045T-6R8N	TDK	6259
				±20%, DCR=100mΩmax, 1.65A	VLF504015MT-6R8M	TDK	5040
				±30%, DCR=54mΩmax, 1.95A	B1079AS-4R7N (DS73LC)	TOKO	7676
				±20%, DCR=44.6mΩmax, 5.5A	IHLP2525EZER6R8M01	VISHAY	6965
				±30%, DCR=45mΩmax, 1.7A	744053006 (WE-TPC 5828)	WÜRTH	5858
1	R3	Resistor	24kΩ	0.063W, 50V, 5%	MCR01MZPJ243	ROHM	1005
1	R4	Resistor	430kΩ	0.063W, 50V, 1%	MCR01MZPF4303	ROHM	1005
1	R5	Resistor	82kΩ	0.063W, 50V, 1%	MCR01MZPF8202	ROHM	1005
1	U1	IC	-	Buck DC/DC Converter	BD9E102FJ	ROHM	SOP-J8

### Precautions for use

- (1) This document provides the BOM for evaluation boards. Small parts can also be selected for resistor, capacitor, and coil.
- (2) When miniaturizing a resistor, consider decrease in rated power and withstand voltage.
- (3) When miniaturizing a ceramic capacitor, consider decrease in withstand voltage. In addition, the capacity may be decreased by DC bias characteristics, and the desired characteristics may not be obtained.
- (4) If ceramic capacitor models differ even when they have the same capacity and withstand voltage, the capacity may be decreased by DC bias characteristics depending on the model, and desired characteristics may not be obtained. Be sure to check the DC bias characteristics.
- (5) When miniaturizing a coil, consider increase in direct current resistance and decrease in rated current. An increase in DC resistance can cause a deterioration of power conversion efficiency. A decrease in rated current can saturate the coil when outputting a large current, which may deteriorate efficiency or make it impossible to obtain the desired output current.
- (6) If there is a possibility that the output will short-circuit, use a coil with a rated current that is larger than the maximum IC output current. For example, even when up to 100 mA is actually used for an IC that can output 1 A, select a coil whose rated current is larger than 1 A. If a coil with a small rated current is used, it will be saturated by a large current in the event of output short-circuiting, resulting in a steep increase in output voltage. The IC may be broken down because the processing speed of the overcurrent protecting function of the IC cannot keep up with the increase in voltage.
- (7) This circuit constant is the value for our evaluation board. It may be necessary to adjust the constant for the actual board. Carry out suitable evaluations.

#### Notes

- 1) The information contained herein is subject to change without notice.
- Before you use our Products, please contact our sales representative and verify the latest specifications:
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors. Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Poducts beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products specified in this document are not designed to be radiation tolerant.
- 7) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative: transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 8) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 9) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 10) ROHM has used reasonable care to ensur the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 11) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 12) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 13) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.

More detail product informations and catalogs are available, please contact us.

## ROHM Customer Support System

http://www.rohm.com/contact/